

Εθνικό Μετσόβιο Πολυτεχνείο

Σχολή Ηλεκτρολόγων Μηχανικών και Μηχανικών Υπολογιστών

3η Σειρά Ασκήσεων

Μάθημα: Ψηφιακά Συστήματα VLSI

Εξάμηνο: 8^ο

Ονοματεπώνυμο: Αλεξοπούλου Γεωργία, Γκενάκου Ζωή

Θέμα 1: Full Synchronous Adder

Στο πρώτο μέρος της εργαστηριακής άσκησης υλοποιούμε έναν σύγχρονο Πλήρη Αθροιστή (Full Adder - FA) με περιγραφή συμπεριφοράς (Behavioral).

Ένας σύγχρονος πλήρης αθροιστής είναι ένα ψηφιακό κύκλωμα που προσθέτει τρία δυαδικά ψηφία (A, B και Cin) και παράγει ένα άθροισμα (S) και ένα κρατούμενο (Cout). Ο όρος "σύγχρονος" αναφέρεται στο γεγονός ότι όλες οι λειτουργίες εντός του αθροιστή συγχρονίζονται με ένα κοινό σήμα ρολογιού. Αυτό σημαίνει ότι οι είσοδοι δειγματοληπτούνται και υποβάλλονται σε επεξεργασία μόνο σε συγκεκριμένες άκρες ρολογιού (στη δικιά μας περίπτωση στην θετική ακμή), διασφαλίζοντας τον σωστό χρονισμό και τη λειτουργία του κυκλώματος.

Το άθροισμα (S) έξοδος του σύγχρονου πλήρους αθροιστή υπολογίζεται με βάση τα δυαδικά ψηφία εισόδου A, B και το κρατούμενο εισόδου (Cin). Το άθροισμα είναι «1» εάν ο συνολικός αριθμός των «1» μεταξύ των εισόδων (A, B, Cin) είναι περιττός και «0» διαφορετικά.

Η εκτέλεση (Cout) του σύγχρονου πλήρους αθροιστή προσδιορίζεται με βάση τα bit εισόδου A, B και Cin. Είναι «1» εάν τουλάχιστον δύο από τα σήματα εισόδου (A, B, Cin) είναι «1».

Ο κώδικας Behavioral αρχιτεκτονικής φαίνεται παρακάτω:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity full_adder_bh is
    Port ( a : in std_logic;
          b : in std_logic;
          cin : in std_logic;
          clk : in std_logic;
          rst : in std_logic;
          sum : out std_logic;
          cout : out std_logic);
end full_adder_bh;

architecture Behavioral of full_adder_bh is

begin
    process(clk, rst)
    begin
        if rst='0' then
            sum <= '0';
            cout <= '0';
        elsif rising_edge(clk) then
            if((a='1' and b='1' and cin='0') or (a='0' and b='1' and
cin='1') or (a='1' and b='0' and cin='1') or (a='1' and b='1' and
cin='1')) then
                cout <= '1';
            else
                cout <= '0';
            end if;


            if ((a='1' and b='0' and cin='0') or (a='0' and b='1' and
cin='0') or (a='0' and b='0' and cin='1') or (a='1' and b='1' and
cin='1')) then
                sum <= '1';
            else
                sum <= '0';
            end if;
        end if;
    end process;
end architecture Behavioral;

```


end process;

end Behavioral;

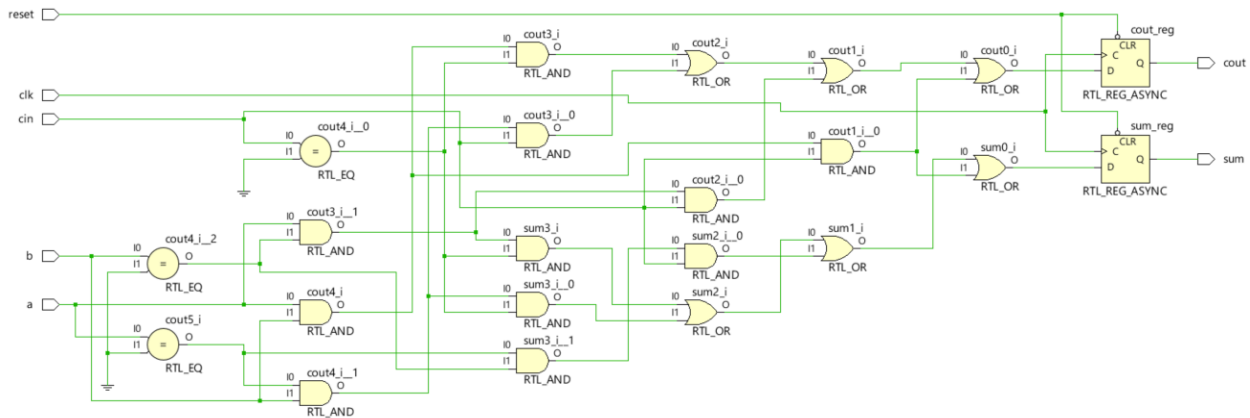To RTL schematic του σύγχρονου πλήρης αθροιστή που υλοποιήσαμε:



To Synthesis Schematic:

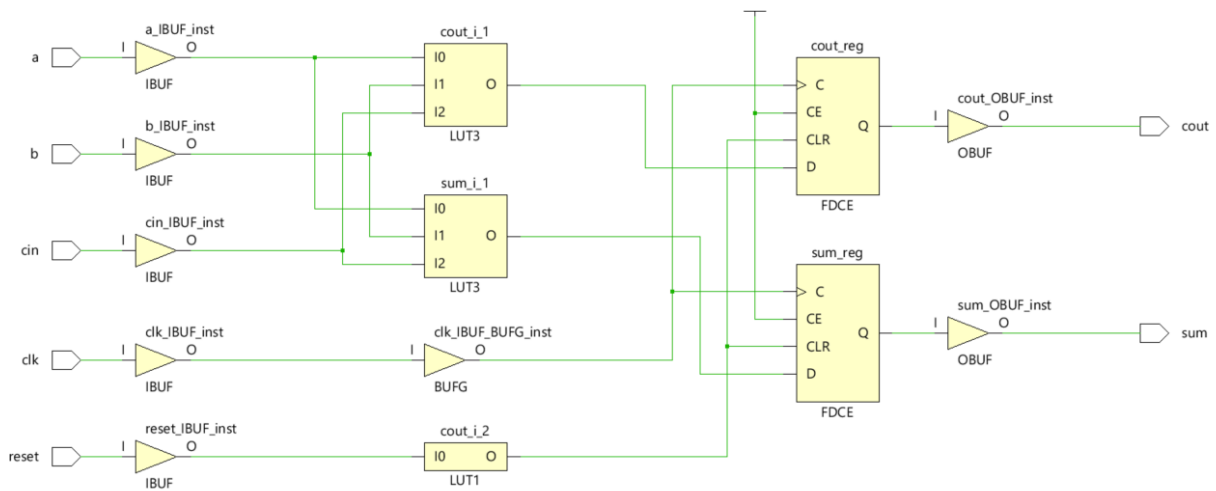

Το critical path ενός ακολουθιακού κυκλώματος, όπως ένας σύγχρονος πλήρης αθροιστής, είναι η μεγαλύτερη διαδρομή από την είσοδο ενός flip-flop στην έξοδο του ίδιου ή άλλου flip-flop. Αντιπροσωπεύει τη μέγιστη καθυστέρηση μέσω του κυκλώματος, η οποία καθορίζει τη μέγιστη συχνότητα λειτουργίας και τη συνολική απόδοση. Το κρίσιμο μονοπάτι του κυκλώματος είναι από τους καταχωρητές cout_reg και sum_reg που αποθηκεύεται το αποτέλεσμα της πρόσθεσης μέχρι την επόμενη

θετική ακμή του ρολογιού προκειμένου να πάει στην έξοδο, μέχρι τις αντίστοιχες εξόδους cout και sum.
Η χρονική του καθυστέρηση είναι 4.076ns:

Name	Slack ^{^1}	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
↳ Path 1	∞	2	2	1	cout_reg/C	cout	4.076	3.276	0.800	∞	
↳ Path 2	∞	2	2	1	sum_reg/C	sum	4.076	3.276	0.800	∞	
↳ Path 3	∞	2	3	2	rst	cout_reg/CLR	2.693	1.106	1.587	∞	input port clock
↳ Path 4	∞	2	3	2	rst	sum_reg/CLR	2.693	1.106	1.587	∞	input port clock
↳ Path 5	∞	2	3	2	b	sum_reg/D	1.932	1.132	0.800	∞	input port clock
↳ Path 6	∞	2	3	2	cin	cout_reg/D	1.906	1.106	0.800	∞	input port clock

Εκτελώντας και την εντολή `report_timing_summary -report_unconstrained` στο terminal παίρνουμε μια πιο αναλυτική αναφορά για το μέγιστο Critical Path:

Max Delay Paths

```
-----
Slack:                inf
Source:               cout_reg/C
                    (rising edge-triggered cell FDCE)
Destination:         cout
                    (output port)
Path Group:           (none)
Path Type:            Max at Slow Process Corner
Data Path Delay:      4.076ns  (logic 3.276ns (80.380%)  route 0.800ns (19.620%))
Logic Levels:         2  (FDCE=1 OBUF=1)

Location              Delay type              Incr(ns)  Path(ns)  Netlist Resource(s)
-----
FDCE                  0.000      0.000 r  cout_reg/C
FDCE (Prop fdce C Q)  0.456      0.456 r  cout_reg/Q

net (fo=1, unplaced)  0.800      1.256   cout_OBUF
OBUF (Prop obuf_I_O)  2.820      4.076 r  cout_OBUF_inst/O
net (fo=0)            0.000      4.076   cout
r cout (OUT)
-----
```

Min Delay Paths

```
-----
Slack:                inf
Source:               a
                    (input port)
Destination:          sum_reg/D
```

Path Group: (none)
 Path Type: Min at Fast Process Corner
 Data Path Delay: 0.590ns (logic 0.253ns (42.882%) route 0.337ns (57.118%))
 Logic Levels: 2 (IBUF=1 LUT3=1)

Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
		0.000	0.000	r a (IN)
net (fo=0)		0.000	0.000	a
IBUF (Prop_ibuf_I_O)		0.211	0.211	r a_IBUF_inst/O
net (fo=2, unplaced)		0.337	0.548	a_IBUF
LUT3 (Prop_lut3_I0_O)		0.042	0.590	r sum_i_1/O
net (fo=1, unplaced)		0.000	0.590	sum0
FDCE				r sum_reg/D

Ο κώδικας για το TestBench φαίνεται παρακάτω:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity full_adder_bh_tb is
-- Port ( );
end full_adder_bh_tb;

architecture bench of full_adder_bh_tb is
  component full_adder_bh is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          cin : in STD_LOGIC;
          clk : in STD_LOGIC;
          rst : in STD_LOGIC;
          sum : out STD_LOGIC;
          cout : out STD_LOGIC);
  end component;

  signal clk_tb, rst_tb, a_tb, b_tb, cin_tb : std_logic := '0';
  signal cout_tb, sum_tb : std_logic;

  constant clock : time := 10ns;

begin
```

```
dut: full_adder_bh
  port map (
    a => a_tb,
    b => b_tb,
    cin => cin_tb,
    clk => clk_tb,
    rst => rst_tb,
    sum => sum_tb,
    cout => cout_tb
  );
```

```
simulation : process
begin
```

```
  rst_tb <= '1';
```

```
  a_tb <= '0';
  b_tb <= '0';
  cin_tb <= '0';
  wait for clock;
```

```
  a_tb <= '0';
  b_tb <= '0';
  cin_tb <= '1';
  wait for clock;
```

```
  a_tb <= '0';
  b_tb <= '1';
  cin_tb <= '0';
  wait for clock;
```

```
  a_tb <= '0';
  b_tb <= '1';
  cin_tb <= '1';
  wait for clock;
```

```
  a_tb <= '1';
  b_tb <= '0';
  cin_tb <= '0';
  wait for clock;
```

```

a_tb <= '1';
b_tb <= '0';
cin_tb <= '1';
wait for clock;

a_tb <= '1';
b_tb <= '1';
cin_tb <= '0';
wait for clock;

a_tb <= '1';
b_tb <= '1';
cin_tb <= '1';
wait for clock;


end process;

generate_clock : process
begin
    clk_tb <= '0';
    wait for clock/2;
    clk_tb <= '1';
    wait for clock/2;
end process;

end bench;

```

To Simulation:

 


Η παραπάνω προσομοίωση επιβεβαιώνει την ορθή λειτουργία του κυκλώματος μας.

Θέμα 2: Synchronous FA with Pipeline

Στο δεύτερο ζητούμενο, πρέπει να υλοποιήσουμε έναν σύγχρονο Αθροιστή διάδοσης κρατούμενου των 4 bits με χρήση της τεχνικής Pipeline. Το κύκλωμα θα πρέπει να τροφοδοτείται με ένα διαφορετικό ζεύγος εισόδων σε κάθε κύκλο ρολογιού και να δίνει αντίστοιχα ορθό αποτέλεσμα σε κάθε κύκλο ρολογιού έπειτα από κάποια αρχική καθυστέρηση Tlatency . Η υλοποίηση να βασιστεί στη δομική μονάδα του Πλήρη Αθροιστή του Ερωτήματος 1 και για τους σκοπούς της άσκησης φτιάχνουμε ένα dff structure για τη διατήρηση τόσο των inputs, όσο και του αντίστοιχου output.

Για να εφαρμόσουμε έναν σύγχρονο αθροιστή διάδοσης κρατούμενου 4 bit χρησιμοποιώντας την τεχνική pipeline, θα χρησιμοποιήσουμε το δομικό στοιχείο Full Adder και θα εισαγάγουμε πρόσθετους καταχωρητές για τη διοχέτευση του υπολογισμού. Αυτή η προσέγγιση μας επιτρέπει να επεξεργαστούμε ένα διαφορετικό ζεύγος εισόδων σε κάθε κύκλο ρολογιού και να δημιουργήσουμε ένα αντίστοιχο αποτέλεσμα σε κάθε κύκλο ρολογιού μετά από μια αρχική καθυστέρηση.

Θα διαθέσουμε 4 σύγχρονους FA του προηγούμενου ερωτήματος, όπου ο κάθε full adder θα δίνει το αποτέλεσμα του στην έξοδο και το κρατούμενο του στον επόμενο FA. Για την ολοκλήρωση της πρόσθεσης δύο αριθμών των 4 bits θα χρειαστεί να περάσουν 4 κύκλοι, κατά την διάρκεια των οποίων ο

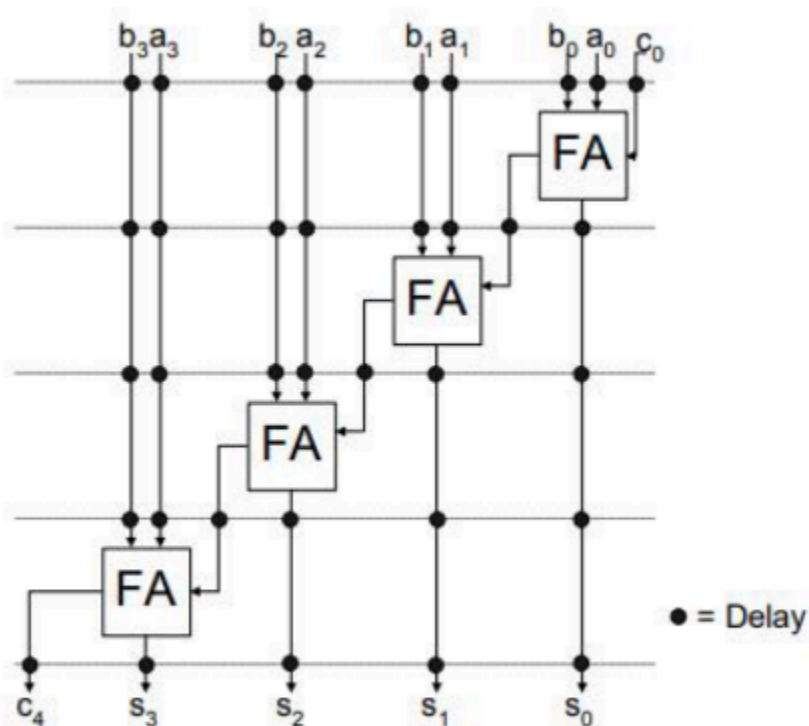

Σχήμα 1.13 Ο αθροιστής διάδοσης κρατούμενου σε λειτουργία συνεχούς διοχέτευσης

κάθε FA θα χρησιμοποιείται διαδοχικά για έναν κύκλο. Αυτό σημαίνει ότι μόλις συμπληρωθεί η πρόσθεση των αντίστοιχων ψηφίων δύο αριθμών από έναν πλήρη αθροιστή, μπορεί να προχωρήσει στον χειρισμό των αντίστοιχων ψηφίων της επόμενης πρόσθεσης. Ωστόσο, για να πραγματοποιηθεί ομαλά αυτή η

μεταβίβαση, το κρατούμενο πρέπει να έχει δημιουργηθεί από τον προηγούμενο αθροιστή. Για να διασφαλίσουμε τον σωστό συγχρονισμό θα ενσωματώσουμε καταχωρητές για την αποθήκευση των bit εισόδου A_i και B_i μέχρι να δημιουργηθεί το κρατούμενο C_{i-1} . Επιπλέον, θα προστεθούν καταχωρητές στην έξοδο κάθε πλήρους αθροιστή για να διασφαλιστεί ότι τα αποτελέσματά του φτάνουν στην έξοδο ταυτόχρονα. Οι καθυστερήσεις που σχετίζονται με αυτούς τους καταχωρητές υποδεικνύονται με τελείες στο παρακάτω διάγραμμα.

Παραθέτουμε τον κώδικα τόσο για το DFF τόσο και για το αθροιστή διάδοσης κρατουμένου:

1) DFF

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity dff is
    Port ( D : in STD_LOGIC;
          clk : in STD_LOGIC;
          rst : in STD_LOGIC;
          Q : out STD_LOGIC);
end dff;

architecture Behavioral of dff is

begin

    process(clk, rst) begin
        if rst='0' then
            Q<='0';
        elsif rising_edge(clk) then
            Q<=D;
        end if;
    end process;

end Behavioral;
```

2) Αθροιστής διάδοσης κρατουμένου

```
library IEEE;
```

```

use IEEE.STD_LOGIC_1164.ALL;

entity full_adder_4bit_pipeline is
    Port ( A : in std_logic_vector (3 downto 0);
           B : in std_logic_vector (3 downto 0);
           Cin : in std_logic;
           Clk : in std_logic;
           Rst : in std_logic;
           Sum : out std_logic_vector (3 downto 0);
           Cout : out std_logic);
end full_adder_4bit_pipeline;

architecture Structural of full_adder_4bit_pipeline is

    component dff is
        Port ( D : in std_logic;
              clk : in std_logic;
              rst : in std_logic;
              Q : out std_logic);
    end component;

    component full_adder_bh is
        Port ( a : in std_logic;
              b : in std_logic;
              cin : in std_logic;
              clk : in std_logic;
              rst : in std_logic;
              sum : out std_logic;
              cout : out std_logic);
    end component;

    --signal regCout, regCin : std_logic_vector(2 downto 0);
    signal c0, c1, c2, dffA0, dffB0, dffS2 : std_logic;
    signal dffA1, dffB1, dffS1 : std_logic_vector(1 downto 0);
    signal dffA2, dffB2, dffS0 : std_logic_vector(2 downto 0);

begin

    FA0: full_adder_bh port map (a=>A(0), b=>B(0), cin=>Cin, clk=>Clk,

```

```

rst=>Rst, sum=>dffS0(0), cout=>c0);
dffS0_0: dff port map (D=>dffS0(0), clk=>clk, rst=>rst, Q=>dffS0(1));
dffS0_1: dff port map (D=>dffS0(1), clk=>clk, rst=>rst, Q=>dffS0(2));
dffS0_2: dff port map (D=>dffS0(2), clk=>clk, rst=>rst, Q=>Sum(0));

regA0_0: dff port map (D=>A(1), clk=>clk, rst=>rst, Q=>dffA0);
regB0_0: dff port map (D=>B(1), clk=>clk, rst=>rst, Q=>dffB0);
FA1: full_adder_bh port map (a=>dffA0, b=>dffB0, cin=>c0, clk=>Clk,
rst=>Rst, sum=>dffS1(0), cout=>c1);
regS1_0: dff port map (D=>dffS1(0), clk=>clk, rst=>rst, Q=>dffS1(1));
regS1_1: dff port map (D=>dffS1(1), clk=>clk, rst=>rst, Q=>Sum(1));


regA1_0: dff port map (D=>A(2), clk=>clk, rst=>rst, Q=>dffA1(0));
regB1_0: dff port map (D=>B(2), clk=>clk, rst=>rst, Q=>dffB1(0));
regA1_1: dff port map (D=>dffA1(0), clk=>clk, rst=>rst, Q=>dffA1(1));
regB1_1: dff port map (D=>dffB1(0), clk=>clk, rst=>rst, Q=>dffB1(1));
FA2: full_adder_bh port map (a=>dffA1(1), b=>dffB1(1), cin=>c1,
clk=>Clk, rst=>Rst, sum=>dffS2, cout=>c2);
regS2_0: dff port map (D=>dffS2, clk=>clk, rst=>rst, Q=>Sum(2));

regA3_0: dff port map (D=>A(3), clk=>clk, rst=>rst, Q=>dffA2(0));
regB3_0: dff port map (D=>B(3), clk=>clk, rst=>rst, Q=>dffB2(0));
regA3_1: dff port map (D=>dffA2(0), clk=>clk, rst=>rst, Q=>dffA2(1));
regB3_1: dff port map (D=>dffB2(0), clk=>clk, rst=>rst, Q=>dffB2(1));
regA3_2: dff port map (D=>dffA2(1), clk=>clk, rst=>rst, Q=>dffA2(2));
regB3_2: dff port map (D=>dffB2(1), clk=>clk, rst=>rst, Q=>dffB2(2));
FA3: full_adder_bh port map (a=>dffA2(2), b=>dffB2(2), cin=>c2,
clk=>Clk, rst=>Rst, sum=>Sum(3), cout=>Cout);


end Structural;

```

To RTL Schematic για τον DFF:

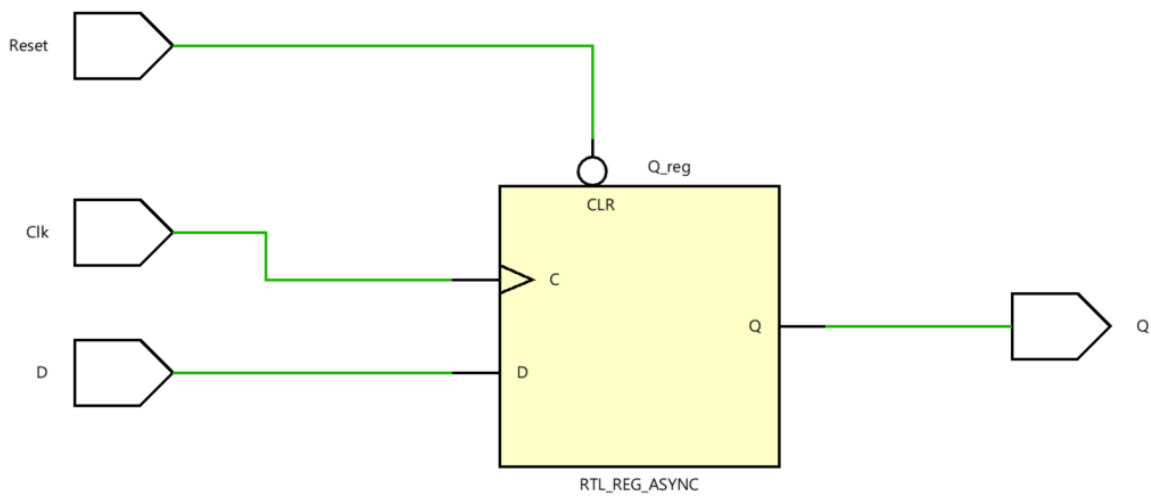


Και το DFF Synthesis Schematic:

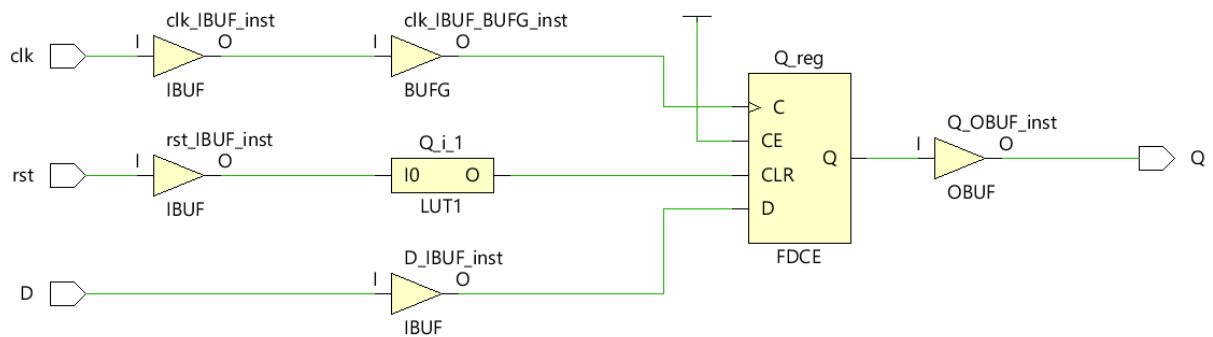

Χρησιμοποιώντας Structural Architecture και αξιοποιώντας τις δομές του Θέματος ένα και του dff, καταλήγουμε στο ζητούμενο.

RTL & Synthesis:

 

Ο κώδικας για το TestBench φαίνεται παρακάτω:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity full_adder_4bit_pipeline_tb is
-- Port ( );
end full_adder_4bit_pipeline_tb;

architecture bench of full_adder_4bit_pipeline_tb is

    constant clk1_period: time := 270ps;

    component full_adder_4bit_pipeline is
        Port ( A : in std_logic_vector (3 downto 0);
              B : in std_logic_vector (3 downto 0);
              Cin : in std_logic;
              Clk : in std_logic;
```

```

        Rst : in std_logic;
        Sum : out std_logic_vector (3 downto 0);
        Cout : out std_logic);
end component;

signal clk_tb, rst_tb, cin_tb : std_logic := '0';
signal cout_tb : std_logic;
signal A_tb, B_tb : std_logic_vector(3 downto 0) := "1111";
signal Sum_tb :std_logic_vector(3 downto 0);

constant clock : time := 10 ps ;

begin
    dut: full_adder_4bit_pipeline
        port map(
            A=>A_tb,
            B=>B_tb,
            Cin => cin_tb,
            Clk=>clk_tb,
            Rst=>rst_tb,
            Sum=>Sum_tb,
            Cout=>cout_tb
        );
    simulation : process
    begin
        for i in 0 to 1 loop
            rst_tb <= not rst_tb;
            for l in 0 to 1 loop
                cin_tb <= not cin_tb;
                for j in 0 to 15 loop
                    A_tb<= A_tb + 1;
                    for k in 0 to 15 loop
                        B_tb <= B_tb + 1;
                        wait for clock;
                    end loop;
                end loop;
            end loop;
        end loop;
        wait;
    end process;
end;

```




```






end process;

generate_clock : process
begin
    clk_tb <= '0';
    wait for clock/2;
    clk_tb <= '1';
    wait for clock/2;
end process;
end bench;

```

To Simulation:

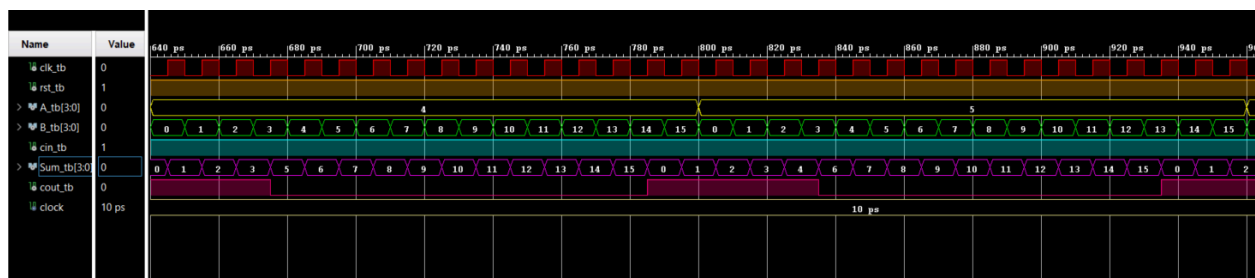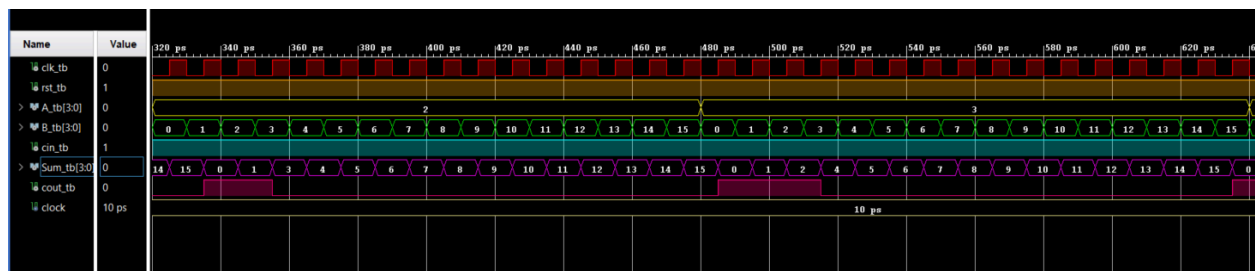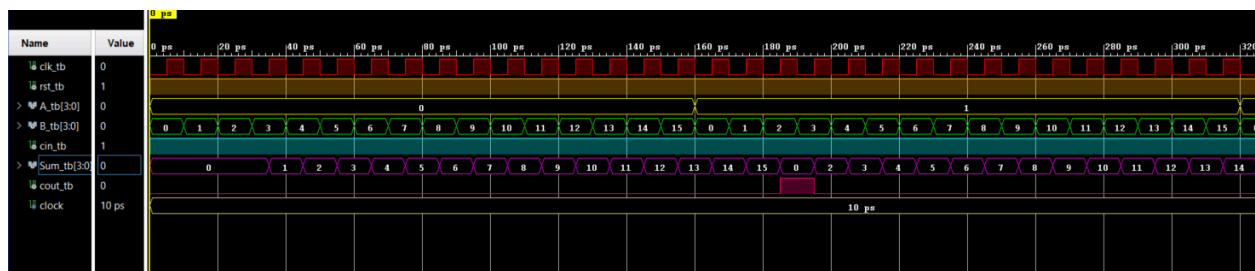

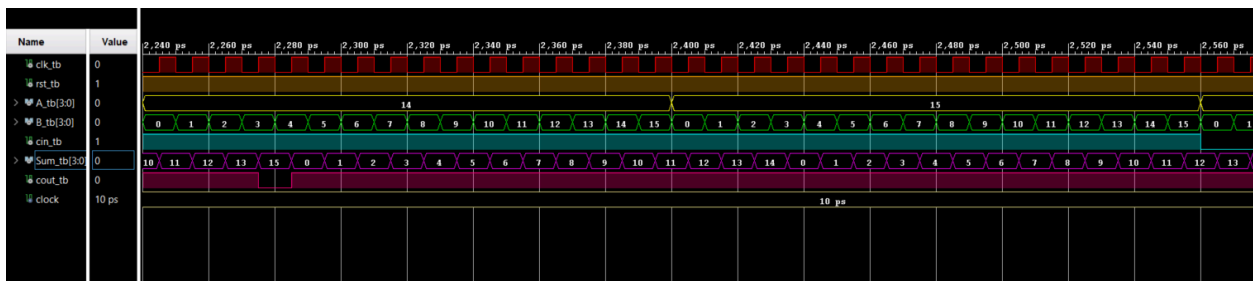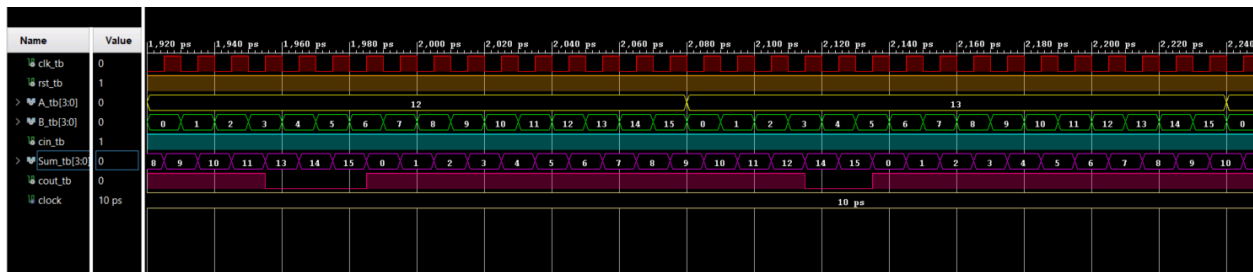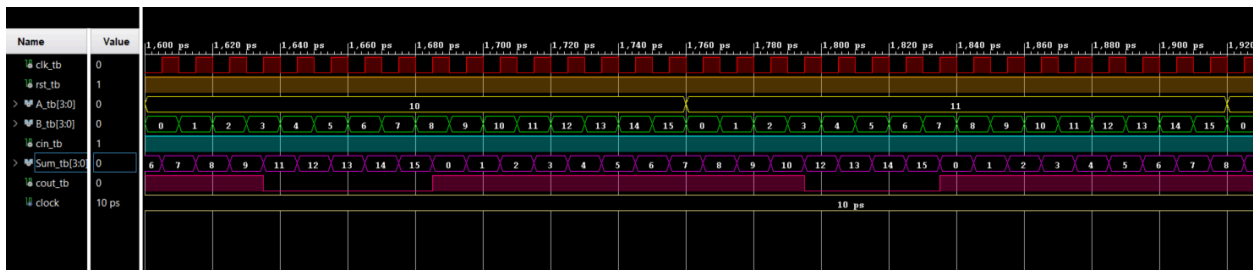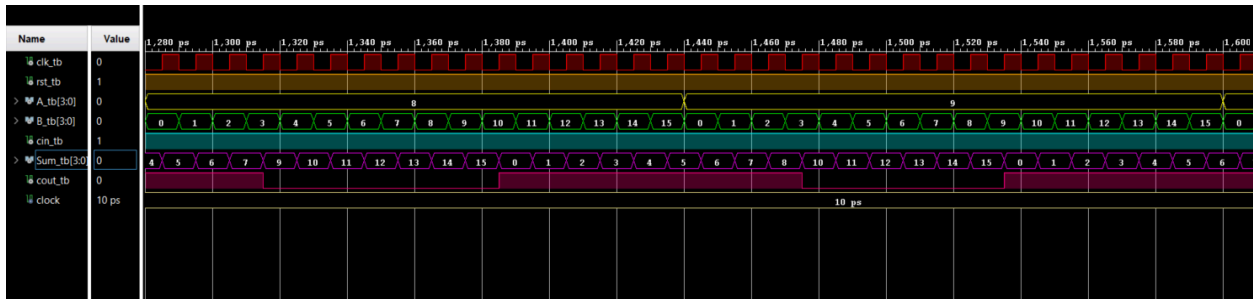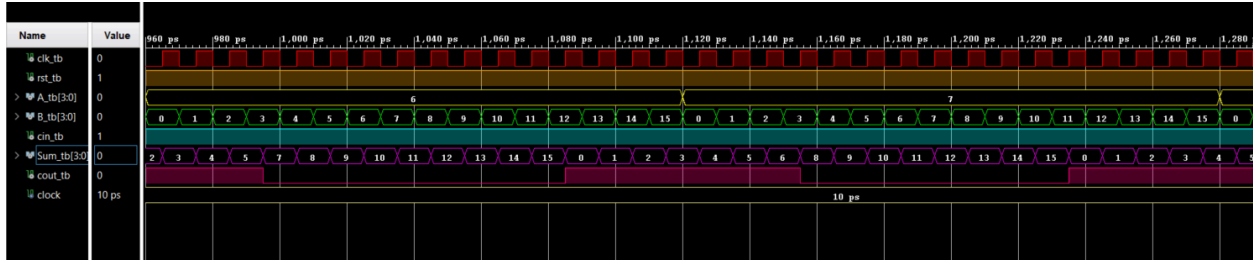

Για το Critical path:

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	Destination Clock	Exception	Clock Uncertainty
Path 1	∞	2	2	1	FA3/cout_reg/C	Cout	4.076	3.276	0.800	∞				0.000
Path 2	∞	2	2	1	dff50_2/Q_reg/C	Sum[0]	4.076	3.276	0.800	∞				0.000
Path 3	∞	2	2	1	reg51_1/Q_reg/C	Sum[1]	4.076	3.276	0.800	∞				0.000
Path 4	∞	2	2	1	reg52_0/Q_reg/C	Sum[2]	4.076	3.276	0.800	∞				0.000
Path 5	∞	2	2	1	FA3/sum_reg/C	Sum[3]	4.076	3.276	0.800	∞				0.000
Path 6	∞	2	3	26	Rst	FA0/cout_reg/CLR	2.748	1.106	1.642	∞	input port clock			0.000
Path 7	∞	2	3	26	Rst	FA0/sum_reg/CLR	2.748	1.106	1.642	∞	input port clock			0.000
Path 8	∞	2	3	26	Rst	FA1/cout_reg/CLR	2.748	1.106	1.642	∞	input port clock			0.000
Path 9	∞	2	3	26	Rst	FA1/sum_reg/CLR	2.748	1.106	1.642	∞	input port clock			0.000
Path 10	∞	2	3	26	Rst	FA2/cout_reg/CLR	2.748	1.106	1.642	∞	input port clock			0.000

Το κρίσιμο μονοπάτι του κυκλώματος είναι για τους 3 πρώτους full adders από το τελευταίο στάδιο καταχωρητών μέχρι το αποτέλεσμα να βγει στην έξοδο και για τον 4ο full adder από την στιγμή που παράγεται το αποτέλεσμα μέχρι να βγει στην έξοδο. Η χρονική καθυστέρηση του κρίσιμου μονοπατιού είναι 4.076ns.

Από την εντολή report_timing_summary -report_unconstrained παίρνουμε πάλι μια πιο αναλυτική αναφορά για το κρίσιμο μονοπάτι.

Max Delay Paths

Slack: inf

Source: FA3/cout_reg/C
(rising edge-triggered cell FDCE)

Destination: Cout
(output port)

Path Group: (none)

Path Type: Max at Slow Process Corner

Data Path Delay: 4.076ns (logic 3.276ns (80.380%) route 0.800ns (19.620%))

Logic Levels: 2 (FDCE=1 OBUF=1)

Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
	FDCE	0.000	0.000	r FA3/cout_reg/C
	FDCE (Prop_fdce_C_Q)	0.456	0.456	r FA3/cout_reg/Q
	net (fo=1, unplaced)	0.800	1.256	Cout_OBUF
	OBUF (Prop_obuf_I_O)	2.820	4.076	r Cout_OBUF_inst/O
	net (fo=0)	0.000	4.076	Cout
				r Cout (OUT)

Min Delay Paths


```

Slack:                inf
Source:               FA0/sum_reg/C
                    (rising edge-triggered cell FDCE)
Destination:         dffs0_0/Q_reg/D
Path Group:           (none)
Path Type:           Min at Fast Process Corner
Data Path Delay:      0.282ns (logic 0.141ns (50.038%) route 0.141ns (49.962%))
Logic Levels:         1 (FDCE=1)
  
```

Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
	FDCE	0.000	0.000	r FA0/sum_reg/C
	FDCE (Prop_fdce_C_Q)	0.141	0.141	r FA0/sum_reg/Q
	net (fo=1, unplaced)	0.141	0.282	dffs0_0/sum
	FDCE			r dffs0_0/Q_reg/D

Η κατανάλωση πόρων είναι η εξής:

Resource	Utilization	Available	Utilization %
LUT	5	17600	0.03
FF	26	35200	0.07
IO	16	100	16.00

 

Συγκρίνουμε την παραπάνω υλοποίηση με τον Παράλληλο Αθροιστή της Εργαστηριακής Άσκησης 2. Για τη δομή αυτή, φαίνονται παρακάτω το critical path και το report timing summary:

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	Destination Clock	Exception	Clock Uncertainty
↳ Path 1	∞	3	4	2	fb	fsum	5.377	3.778	1.599	∞	input port clock			0.000
↳ Path 2	∞	3	4	2	fcin	fcout	5.351	3.752	1.599	∞	input port clock			0.000

Max Delay Paths

```

Slack:          inf
Source:         fb
                (input port)
Destination:    fsum
                (output port)
Path Group:     (none)
Path Type:      Max at Slow Process Corner
Data Path Delay: 5.377ns (logic 3.778ns (70.255%) route 1.599ns (29.745%))
Logic Levels:   3 (IBUF=1 LUT3=1 OBUF=1)
  
```

Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
		0.000	0.000	r fb (IN)
net (fo=0)		0.000	0.000	fb
IBUF (Prop_ibuf_I_O)		0.982	0.982	r fb_IBUF_inst/O
net (fo=2, unplaced)		0.800	1.782	fb_IBUF
LUT3 (Prop_lut3_I1_O)		0.150	1.932	r fsum_OBUF_inst_i_1/O
net (fo=1, unplaced)		0.800	2.732	fsum_OBUF
OBUF (Prop_obuf_I_O)		2.645	5.377	r fsum_OBUF_inst/O
net (fo=0)		0.000	5.377	fsum
				r fsum (OUT)

Min Delay Paths


```

Slack:          inf
Source:         fa
                (input port)
Destination:    fsum
                (output port)
Path Group:     (none)
Path Type:      Min at Fast Process Corner
Data Path Delay: 2.089ns (logic 1.415ns (67.729%) route 0.674ns (32.271%))
Logic Levels:   3 (IBUF=1 LUT3=1 OBUF=1)
  
```

Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
		0.000	0.000	r fa (IN)
net (fo=0)		0.000	0.000	fa
IBUF (Prop_ibuf_I_O)		0.211	0.211	r fa_IBUF_inst/O
net (fo=2, unplaced)		0.337	0.548	fa_IBUF
LUT3 (Prop_lut3_I0_O)		0.042	0.590	r fsum_OBUF_inst_i_1/O
net (fo=1, unplaced)		0.337	0.927	fsum_OBUF
OBUF (Prop_obuf_I_O)		1.162	2.089	r fsum_OBUF_inst/O
net (fo=0)		0.000	2.089	fsum
				r fsum (OUT)

Η κατανάλωση πόρων του Πλήρους Αθροιστή είναι η εξής:

Resource	Utilization	Available	Utilization %
LUT	1	17600	0.01
IO	5	100	5.00

 

Η περίοδος του παράλληλου αθροιστή με pipeline είναι μικρότερη σε σύγκριση με την έκδοση χωρίς pipeline λόγω της εγγενούς αρχιτεκτονικής του pipeline. Στον non-pipelined αθροιστή, κάθε στάδιο του υπολογισμού πρέπει να ολοκληρωθεί πριν περάσουν τα δεδομένα στο επόμενο στάδιο, προκαλώντας μια καθυστέρηση που παρατείνει τον συνολικό χρόνο επεξεργασίας. Αντίθετα, στον pipelined παράλληλο αθροιστή, το κρίσιμο μονοπάτι περιλαμβάνει κυρίως τη διάδοση δεδομένων μεταξύ καταχωρητών μέσα σε διαδοχικά στάδια, με αποτέλεσμα ένα χαμηλότερο όριο στην περίοδο του ρολογιού. Αυτό συμβαίνει επειδή η pipeline προσέγγιση επιτρέπει την ταυτόχρονη επεξεργασία διαφορετικών σταδίων, μειώνοντας τη συνολική καθυστέρηση.


Θεωρώντας τον παράλληλο αθροιστή με σωλήνωση ως σύγχρονο κύκλωμα, η καθυστέρηση κατά μήκος της κρίσιμης διαδρομής καθορίζει την ελάχιστη περίοδο ρολογιού που απαιτείται για τη σωστή λειτουργία. Αυτή η καθυστέρηση, που συμβαίνει μεταξύ διαδοχικών κύκλων ρολογιού, είναι εγγενώς μικρότερη από τον συνολικό χρόνο υπολογισμού που απαιτείται από τον αθροιστή χωρίς σωλήνωση.

Επιπλέον, η σχεδίαση με σωλήνωση απαιτεί πρόσθετους πόρους υλικού, όπως flip-flops για καταχωρητές και ένα παγκόσμιο buffer ρολογιού. Επιπλέον, η εφαρμογή πλήρους αθροιστές ως διαδοχικά σύγχρονα κυκλώματα και στα δύο σχέδια συμβάλλει στην αυξημένη κατανάλωση πόρων όσον αφορά τα στοιχεία flip-flops, πίνακες αναζήτησης (LUT) και στοιχεία εισόδου/εξόδου (IO). Ως εκ τούτου, ο παράλληλος αθροιστής με pipeline καταναλώνει περισσότερους πόρους λόγω της αρχιτεκτονικής του πολυπλοκότητας και της ανάγκης για πρόσθετα εξαρτήματα για την υποστήριξη του pipelining.

Θέμα 3: Synchronous FA with Pipeline

Για τον συστολικό πολλαπλασιαστή διάδοσης κρατούμενων των 4 bits, χρησιμοποιούμε επιπλέον

 καταχωρητές έτσι ώστε οι είσοδοι για την κάθε δομική μονάδα να φτάνουν ταυτόχρονα στους κατάλληλους κύκλους ρολογιού όπως φαίνεται στο διπλανό σχήμα, ώστε να υπολογίζουμε ορθά το αποτέλεσμα. Επιπλέον, χρησιμοποιούμε καταχωρητές, ώστε όλα τα bit του τελικού



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity full_adder_sys_pipeline is
    Port ( a : in std_logic;
          b : in std_logic;
          cin : in std_logic;
          sin : in std_logic;
          clk : in std_logic;
          rst : in std_logic;
          sout : out std_logic;
```

```

        cout : out std_logic;
        D_horizontal : out std_logic;
        D_diagonal : out std_logic);
end full_adder_sys_pipeline;

```

architecture Structural of full_adder_sys_pipeline is

```

    component full_adder_bh is
        Port ( a : in std_logic;
              b : in std_logic;
              cin : in std_logic;
              clk : in std_logic;
              rst : in std_logic;
              sum : out std_logic;
              cout : out std_logic);
    end component;

    component dff is
        Port ( D : in std_logic;
              clk : in std_logic;
              rst : in std_logic;
              Q : out std_logic);
    end component;

    signal dff0, dff1 : std_logic;


begin

    dff0 <= (a and b);
    dff_horizontal : dff port map (D=>b, clk=>clk, rst=>rst,
Q=>D_horizontal);
    dff_diagonal_1 : dff port map (D=>a, clk=>clk, rst=>rst,
Q=>dff1);
    dff_diagonal_2 : dff port map (D=>dff1, clk=>clk, rst=>rst,
Q=>D_diagonal);
    dff_adder : full_adder_bh port map (a=>dff0, b=>sin, cin=>cin,
clk=>clk, rst=>rst, sum=>sout, cout=>cout);

```

```
end Structural;
```

RTL & Synthesis:

 

Ενώ για τον Ripple carry multiplier:

Structural Architecture:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity mult_4bit_pipeline is
    Port ( A : in std_logic_vector (3 downto 0);
          B : in std_logic_vector (3 downto 0);
          clk : in std_logic;
```

```

        rst : in std_logic;
        Pout : out std_logic_vector (7 downto 0));
end mult_4bit_pipeline;

```

architecture Structural of mult_4bit_pipeline is

component full_adder_sys_pipeline is

```

    Port ( a : in std_logic;
           b : in std_logic;
           cin : in std_logic;
           sin : in std_logic;
           clk : in std_logic;
           rst : in std_logic;
           sout : out std_logic;
           cout : out std_logic;
           D_horizontal : out std_logic;
           D_diagonal : out std_logic);
end component;

```

component dff is

```

    Port ( D : in std_logic;
           clk : in std_logic;
           rst : in std_logic;
           Q : out std_logic);
end component;

```

```

    signal result_first_row, carry_first_row, horizontal_first_row,
    diagonal_first_row : std_logic_vector(3 downto 0);
    signal carry_buf_first_row, carry_buf_second_row,
    carry_buf_third_row : std_logic;
    signal result_second_row, carry_second_row,
    horizontal_second_row, diagonal_second_row : std_logic_vector(3
    downto 0);
    signal result_third_row, carry_third_row, horizontal_third_row,
    diagonal_third_row : std_logic_vector(3 downto 0);
    signal dffP0 : std_logic_vector(8 downto 0);
    signal carry_fourth_row, horizontal_fourth_row :
    std_logic_vector(3 downto 0);
    signal dontcare : std_logic;

```



```
signal b1_buf: std_logic_vector(1 downto 0);
signal b2_buf: std_logic_vector(3 downto 0);
signal b3_buf: std_logic_vector(5 downto 0);
```

```
signal dffP1 : std_logic_vector(6 downto 0);
signal dffP2 : std_logic_vector(4 downto 0);
signal dffP3 : std_logic_vector(2 downto 0);
signal dffP4 : std_logic_vector(1 downto 0);
signal dffP5 : std_logic;
```

```
signal a1_buf: std_logic;
signal a2_buf: std_logic_vector(1 downto 0);
signal a3_buf: std_logic_vector(2 downto 0);
```

```
begin
```

```
FIRST_ROW_FIRST: full_adder_sys_pipeline port map(a=>A(0), b=>B(0),
cin=>'0', sin=>'0', clk=>clk, rst=>rst, sout=>dffP0(0),
cout=>carry_first_row(0), D_horizontal=>horizontal_first_row(0),
D_diagonal=>diagonal_first_row(0));
```

```
dffA1_0: dff port map (D=>A(1), clk=>clk, rst=>rst, Q=>a1_buf);
```

```
FIRST_ROW_SECOND: full_adder_sys_pipeline port map(a=>a1_buf,
b=>horizontal_first_row(0), cin=>carry_first_row(0), sin=>'0',
clk=>clk, rst=>rst, sout=>result_first_row(1),
cout=>carry_first_row(1), D_horizontal=>horizontal_first_row(1),
D_diagonal=>diagonal_first_row(1));
```

```
dffA2_0: dff port map (D=>A(2), clk=>clk, rst=>rst, Q=>a2_buf(0));
dffA2_1: dff port map (D=>a2_buf(0), clk=>clk, rst=>rst,
Q=>a2_buf(1));
```

```
FIRST_ROW_THIRD: full_adder_sys_pipeline port map(a=>a2_buf(1),
b=>horizontal_first_row(1), cin=>carry_first_row(1), sin=>'0',
clk=>clk, rst=>rst, sout=>result_first_row(2),
cout=>carry_first_row(2), D_horizontal=>horizontal_first_row(2),
D_diagonal=>diagonal_first_row(2));
```

```
dffA3_0: dff port map (D=>A(3), clk=>clk, rst=>rst, Q=>a3_buf(0));
dffA3_1: dff port map (D=>a3_buf(0), clk=>clk, rst=>rst,
Q=>a3_buf(1));
dffA3_2: dff port map (D=>a3_buf(1), clk=>clk, rst=>rst,
Q=>a3_buf(2));
```

```
FIRST_ROW_FOURTH: full_adder_sys_pipeline port map(a=>a3_buf(2),
b=>horizontal_first_row(2), cin=>carry_first_row(2), sin=>'0',
clk=>clk, rst=>rst, sout=>result_first_row(3),
cout=>carry_first_row(3), D_horizontal=>horizontal_first_row(3),
D_diagonal=>diagonal_first_row(3));
```

```
dffCoutFirstRow: dff port map (D=>carry_first_row(3), clk=>clk,
rst=>rst, Q=>carry_buf_first_row);
```

```
dffP0_0: dff port map (D=>dffP0(0), clk=>clk, rst=>rst, Q=>dffP0(1));
dffP0_1: dff port map (D=>dffP0(1), clk=>clk, rst=>rst, Q=>dffP0(2));
dffP0_2: dff port map (D=>dffP0(2), clk=>clk, rst=>rst, Q=>dffP0(3));
dffP0_3: dff port map (D=>dffP0(3), clk=>clk, rst=>rst, Q=>dffP0(4));
dffP0_4: dff port map (D=>dffP0(4), clk=>clk, rst=>rst, Q=>dffP0(5));
dffP0_5: dff port map (D=>dffP0(5), clk=>clk, rst=>rst, Q=>dffP0(6));
dffP0_6: dff port map (D=>dffP0(6), clk=>clk, rst=>rst, Q=>dffP0(7));
dffP0_7: dff port map (D=>dffP0(7), clk=>clk, rst=>rst, Q=>dffP0(8));
dffP0_8: dff port map (D=>dffP0(8), clk=>clk, rst=>rst, Q=>Pout(0));
```

```
dffB1_0: dff port map (D=>B(1), clk=>clk, rst=>rst, Q=>b1_buf(0));
dffB1_1: dff port map (D=>b1_buf(0), clk=>clk, rst=>rst,
Q=>b1_buf(1));
```

```
SECOND_ROW_FIRST: full_adder_sys_pipeline port
map(a=>diagonal_first_row(0), b=>b1_buf(1), cin=>'0',
sin=>result_first_row(1), clk=>clk, rst=>rst, sout=>dffP1(0),
cout=>carry_second_row(0), D_horizontal=>horizontal_second_row(0),
D_diagonal=>diagonal_second_row(0));
```

```
SECOND_ROW_SECOND: full_adder_sys_pipeline port
map(a=>diagonal_first_row(1), b=>horizontal_second_row(0),
cin=>carry_second_row(0), sin=>result_first_row(2), clk=>clk,
rst=>rst, sout=>result_second_row(1), cout=>carry_second_row(1),
```

```

D_horizontal=>horizontal_second_row(1),
D_diagonal=>diagonal_second_row(1));
SECOND_ROW_THIRD: full_adder_sys_pipeline port
map(a=>diagonal_first_row(2), b=>horizontal_second_row(1),
cin=>carry_second_row(1), sin=>result_first_row(3), clk=>clk,
rst=>rst, sout=>result_second_row(2), cout=>carry_second_row(2),
D_horizontal=>horizontal_second_row(2),
D_diagonal=>diagonal_second_row(2));
SECOND_ROW_FOURTH: full_adder_sys_pipeline port
map(a=>diagonal_first_row(3), b=>horizontal_second_row(2),
cin=>carry_second_row(2), sin=>carry_buf_first_row, clk=>clk,
rst=>rst, sout=>result_second_row(3), cout=>carry_second_row(3),
D_horizontal=>horizontal_second_row(3),
D_diagonal=>diagonal_second_row(3));

dffCoutSecondRow: dff port map (D=>carry_second_row(3), clk=>clk,
rst=>rst, Q=>carry_buf_second_row);

dffP1_0: dff port map (D=>dffP1(0), clk=>clk, rst=>rst, Q=>dffP1(1));
dffP1_1: dff port map (D=>dffP1(1), clk=>clk, rst=>rst, Q=>dffP1(2));
dffP1_2: dff port map (D=>dffP1(2), clk=>clk, rst=>rst, Q=>dffP1(3));
dffP1_3: dff port map (D=>dffP1(3), clk=>clk, rst=>rst, Q=>dffP1(4));
dffP1_4: dff port map (D=>dffP1(4), clk=>clk, rst=>rst, Q=>dffP1(5));
dffP1_5: dff port map (D=>dffP1(5), clk=>clk, rst=>rst, Q=>dffP1(6));
dffP1_6: dff port map (D=>dffP1(6), clk=>clk, rst=>rst, Q=>Pout(1));

dffB2_0: dff port map (D=>B(2), clk=>clk, rst=>rst, Q=>b2_buf(0));
dffB2_1: dff port map (D=>b2_buf(0), clk=>clk, rst=>rst,
Q=>b2_buf(1));
dffB2_2: dff port map (D=>b2_buf(1), clk=>clk, rst=>rst,
Q=>b2_buf(2));
dffB2_3: dff port map (D=>b2_buf(2), clk=>clk, rst=>rst,
Q=>b2_buf(3));

THIRD_ROW_FIRST: full_adder_sys_pipeline port
map(a=>diagonal_second_row(0), b=>b2_buf(3), cin=>'0',
sin=>result_second_row(1), clk=>clk, rst=>rst, sout=>dffP2(0),
cout=>carry_third_row(0), D_horizontal=>horizontal_third_row(0),
D_diagonal=>diagonal_third_row(0));

```

```

THIRD_ROW_SECOND: full_adder_sys_pipeline port
map(a=>diagonal_second_row(1), b=>horizontal_third_row(0),
cin=>carry_third_row(0), sin=>result_second_row(2), clk=>clk,
rst=>rst, sout=>result_third_row(1), cout=>carry_third_row(1),
D_horizontal=>horizontal_third_row(1),
D_diagonal=>diagonal_third_row(1));
THIRD_ROW_THIRD: full_adder_sys_pipeline port
map(a=>diagonal_second_row(2), b=>horizontal_third_row(1),
cin=>carry_third_row(1), sin=>result_second_row(3), clk=>clk,
rst=>rst, sout=>result_third_row(2), cout=>carry_third_row(2),
D_horizontal=>horizontal_third_row(2),
D_diagonal=>diagonal_third_row(2));
THIRD_ROW_FOURTH: full_adder_sys_pipeline port
map(a=>diagonal_second_row(3), b=>horizontal_third_row(2),
cin=>carry_third_row(2), sin=>carry_buf_second_row, clk=>clk,
rst=>rst, sout=>result_third_row(3), cout=>carry_third_row(3),
D_horizontal=>horizontal_third_row(3),
D_diagonal=>diagonal_third_row(3));

```

```

dffCoutThirdRow: dff port map (D=>carry_third_row(3), clk=>clk,
rst=>rst, Q=>carry_buf_third_row);

```

```

dffP2_0: dff port map (D=>dffP2(0), clk=>clk, rst=>rst, Q=>dffP2(1));
dffP2_1: dff port map (D=>dffP2(1), clk=>clk, rst=>rst, Q=>dffP2(2));
dffP2_2: dff port map (D=>dffP2(2), clk=>clk, rst=>rst, Q=>dffP2(3));
dffP2_3: dff port map (D=>dffP2(3), clk=>clk, rst=>rst, Q=>dffP2(4));
dffP2_4: dff port map (D=>dffP2(4), clk=>clk, rst=>rst, Q=>Pout(2));

```

```

dffB3_0: dff port map (D=>B(3), clk=>clk, rst=>rst, Q=>b3_buf(0));
dffB3_1: dff port map (D=>b3_buf(0), clk=>clk, rst=>rst,
Q=>b3_buf(1));
dffB3_2: dff port map (D=>b3_buf(1), clk=>clk, rst=>rst,
Q=>b3_buf(2));
dffB3_3: dff port map (D=>b3_buf(2), clk=>clk, rst=>rst,
Q=>b3_buf(3));
dffB3_4: dff port map (D=>b3_buf(3), clk=>clk, rst=>rst,
Q=>b3_buf(4));
dffB3_5: dff port map (D=>b3_buf(4), clk=>clk, rst=>rst,
Q=>b3_buf(5));

```

```

FOURTH_ROW_FIRST: full_adder_sys_pipeline port
map(a=>diagonal_third_row(0), b=>b3_buf(5), cin=>'0',
sin=>result_third_row(1), clk=>clk, rst=>rst, sout=>dffP3(0),
cout=>carry_fourth_row(0), D_horizontal=>horizontal_fourth_row(0),
D_diagonal=>dontcare);

dffP3_0: dff port map (D=>dffP3(0), clk=>clk, rst=>rst, Q=>dffP3(1));
dffP3_1: dff port map (D=>dffP3(1), clk=>clk, rst=>rst, Q=>dffP3(2));
dffP3_2: dff port map (D=>dffP3(2), clk=>clk, rst=>rst, Q=>Pout(3));

FOURTH_ROW_SECOND: full_adder_sys_pipeline port
map(a=>diagonal_third_row(1), b=>horizontal_fourth_row(0),
cin=>carry_fourth_row(0), sin=>result_third_row(2), clk=>clk,
rst=>rst, sout=>dffP4(0), cout=>carry_fourth_row(1),
D_horizontal=>horizontal_fourth_row(1), D_diagonal=>dontcare);

dffP4_0: dff port map (D=>dffP4(0), clk=>clk, rst=>rst, Q=>dffP4(1));
dffP4_1: dff port map (D=>dffP4(1), clk=>clk, rst=>rst, Q=>Pout(4));

FOURTH_ROW_THIRD: full_adder_sys_pipeline port
map(a=>diagonal_third_row(2), b=>horizontal_fourth_row(1),
cin=>carry_fourth_row(1), sin=>result_third_row(3), clk=>clk,
rst=>rst, sout=>dffP5, cout=>carry_fourth_row(2),
D_horizontal=>horizontal_fourth_row(2), D_diagonal=>dontcare);


dffP5_0: dff port map (D=>dffP5, clk=>clk, rst=>rst, Q=>Pout(5));

FOURTH_ROW_FOURTH: full_adder_sys_pipeline port
map(a=>diagonal_third_row(3), b=>horizontal_fourth_row(2),
cin=>carry_fourth_row(2), sin=>carry_buf_third_row, clk=>clk,
rst=>rst, sout=>Pout(6), cout=>Pout(7),
D_horizontal=>horizontal_fourth_row(3), D_diagonal=>dontcare);

end Structural;

```

RTL & Synthesis:

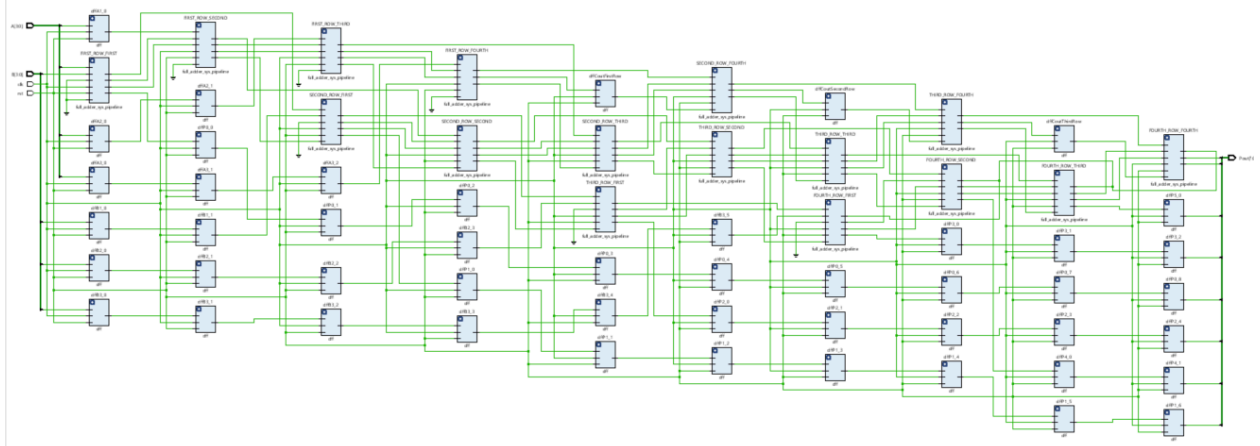

Ο κώδικας για το Testbench:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_unsigned.all;

entity mult_4bit_pipeline_tb is
-- Port()
end mult_4bit_pipeline_tb;

architecture bench of mult_4bit_pipeline_tb is

    component mult_4bit_pipeline is
        Port ( A : in std_logic_vector (3 downto 0);
              B : in std_logic_vector (3 downto 0);
              clk : in std_logic;
              rst : in std_logic;
              Pout : out std_logic_vector (7 downto 0));
    end component;

    signal A_tb, B_tb : std_logic_vector (3 downto 0) := "1111";
    signal clk_tb, rst_tb : std_logic := '0';
    signal Pout_tb : std_logic_vector (7 downto 0);

    constant clock : time := 10 ps;
```

```

begin
    dut : mult_4bit_pipeline
        port map (
            A=>A_tb,
            B=>B_tb,
            clk=>clk_tb,
            rst=>rst_tb,
            Pout=>Pout_tb
        );




    simulation : process
    begin
        for i in 0 to 1 loop
            rst_tb <= not rst_tb;
            for j in 0 to 15 loop
                A_tb<=A_tb + 1;
                for k in 0 to 15 loop
                    B_tb<=B_tb + 1;
                    wait for clock;
                end loop;
            end loop;
            wait for 10*clock;
        end loop;
    end process;

    generate_clock : process
    begin
        clk_tb <= '0';
        wait for clock/2;
        clk_tb <= '1';
        wait for clock/2;
    end process;

end bench;

```

Simulation:

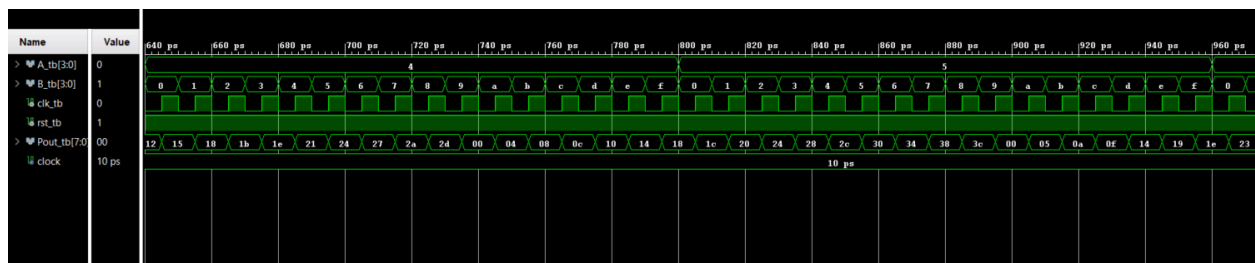  

Η αρχική καθυστέρηση, που ονομάζεται Latency, είναι 10 κύκλοι ρολογιού πριν ο πρώτος πολλαπλασιασμός δώσει ένα αποτέλεσμα, το οποίο εκτείνεται επίσης σε 10 κύκλους. Στη συνέχεια, λόγω της εφαρμογής τεχνικής συστολικής σωλήνωσης, κάθε κύκλος ρολογιού παράγει ένα σωστό αποτέλεσμα για τον αντίστοιχο πολλαπλασιασμό. Σε αυτή την τεχνική, το σύστημα χρησιμοποιεί αποτελεσματικά πόρους επεξεργάζοντας δεδομένα με συγχρονισμένο και συνεχή τρόπο σε πολλαπλά στοιχεία επεξεργασίας.

Οι συστολικές συστοιχίες, που συχνά χρησιμοποιούνται σε τέτοιες τεχνικές διοχέτευσης, διευκολύνουν την παράλληλη επεξεργασία δεδομένων μέσω διασυνδεδεμένων στοιχείων επεξεργασίας. Κάθε στοιχείο εκτελεί μια συγκεκριμένη λειτουργία στα δεδομένα και μεταβιβάζει το αποτέλεσμα στο επόμενο στοιχείο, επιτρέποντας μια βελτιωμένη ροή υπολογισμών. Σε αυτό το πλαίσιο, η καθυστέρηση των 10 κύκλων επιτρέπει τη διάδοση των απαραίτητων εισροών μέσω του pipeline, διασφαλίζοντας ότι μέχρι τη στιγμή που το τελευταίο δομικό στοιχείο υπολογίζει το αποτέλεσμα στον 10ο κύκλο, όλες οι απαιτούμενες εισροές έχουν υποστεί σωστή επεξεργασία μέσω των προηγούμενων μπλοκ. Αυτή η συγχρονισμένη προσέγγιση ελαχιστοποιεί τον χρόνο αδράνειας και μεγιστοποιεί τη χρήση των πόρων, με αποτέλεσμα την αποδοτική υπολογιστική απόδοση.

Το Critical path του κυκλώματος είναι από τους τελικούς καταχωρητές ή της δομική μονάδα που χρησιμοποιείται στον τελευταίο κύκλο μέχρι την έξοδο. Η χρονική καθυστέρηση είναι 4.076ns.

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	De
↳ Path 1	∞	2	2	1	dffP0_8/Q_reg/C	Pout[0]	4.076	3.276	0.800	∞		
↳ Path 2	∞	2	2	1	dffP1_6/Q_reg/C	Pout[1]	4.076	3.276	0.800	∞		
↳ Path 3	∞	2	2	1	dffP2_4/Q_reg/C	Pout[2]	4.076	3.276	0.800	∞		
↳ Path 4	∞	2	2	1	dffP3_2/Q_reg/C	Pout[3]	4.076	3.276	0.800	∞		
↳ Path 5	∞	2	2	1	dffP4_1/Q_reg/C	Pout[4]	4.076	3.276	0.800	∞		
↳ Path 6	∞	2	2	1	dffP5_0/Q_reg/C	Pout[5]	4.076	3.276	0.800	∞		
↳ Path 7	∞	2	2	1	FOURTH_ROW_sum_reg/C	Pout[6]	4.076	3.276	0.800	∞		
↳ Path 8	∞	2	2	1	FOURTH_ROW_cout_reg/C	Pout[7]	4.076	3.276	0.800	∞		
↳ Path 9	∞	2	3	88	rst	FIRST_ROW_F..._reg_c/CLR	2.778	1.106	1.672	∞	input port clock	
↳ Path 10	∞	2	3	88	rst	FIRST_ROW_.../Q_reg/CLR	2.778	1.106	1.672	∞	input port clock	

Πιο αναλυτικά το βλέπουμε και εκτελώντας την εντολή `report_timing_summary -report_unconstrained` :

Max Delay Paths

Slack:	inf			
Source:	dffP0_8/Q_reg/C (rising edge-triggered cell FDCE)			
Destination:	Pout[0] (output port)			
Path Group:	(none)			
Path Type:	Max at Slow Process Corner			
Data Path Delay:	4.076ns (logic 3.276ns (80.380%) route 0.800ns (19.620%))			
Logic Levels:	2 (FDCE=1 OBUF=1)			
Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
	FDCE	0.000	0.000	r dffP0_8/Q_reg/C
	FDCE (Prop_fdce_C_Q)	0.456	0.456	r dffP0_8/Q_reg/Q
	net (fo=1, unplaced)	0.800	1.256	Pout_OBUF[0]
	OBUF (Prop_obuf_I_O)	2.820	4.076	r Pout_OBUF[0]_inst/O
	net (fo=0)	0.000	4.076	Pout[0]
				r Pout[0] (OUT)

Min Delay Paths

Slack:	inf			
Source:	FIRST_ROW_FIRST/dff_diagonal_1/Q_reg/C (rising edge-triggered cell FDCE)			
Destination:	FIRST_ROW_FIRST/dff_diagonal_2/Q_reg/D (none)			
Path Group:	(none)			
Path Type:	Min at Fast Process Corner			
Data Path Delay:	0.282ns (logic 0.141ns (50.038%) route 0.141ns (49.962%))			
Logic Levels:	1 (FDCE=1)			
Location	Delay type	Incr(ns)	Path(ns)	Netlist Resource(s)
	FDCE	0.000	0.000	r FIRST_ROW_FIRST/dff_diagonal_1/Q_reg/C
	FDCE (Prop_fdce_C_Q)	0.141	0.141	r FIRST_ROW_FIRST/dff_diagonal_1/Q_reg/Q
	net (fo=1, unplaced)	0.141	0.282	FIRST_ROW_FIRST/dff_diagonal_2/Q
	FDCE			r FIRST_ROW_FIRST/dff_diagonal_2/Q_reg/D